

SR Latch - Complete Summary

Your Name

July 2, 2025

1 Introduction

An **SR Latch (Set-Reset Latch)** is a basic **bistable** (two stable states) sequential circuit that stores **1 bit** of data. It is constructed using **cross-coupled NOR gates** or **NAND gates**, forming a feedback loop to maintain its state.

2 Types of SR Latches

- **NOR-based SR Latch**
- **NAND-based SR Latch** (also called **SR Latch with active-low inputs**)

3 NOR-based SR Latch

3.1 Structure

Two NOR gates with feedback.

3.2 Inputs

- **S (Set)** – Sets output $Q = 1$
- **R (Reset)** – Resets output $Q = 0$

3.3 Truth Table

S	R	Q	Q'	State
0	0	Q	Q'	Hold (Memory)
1	0	1	0	Set ($Q = 1$)
0	1	0	1	Reset ($Q = 0$)
1	1	0	0	Invalid (Race)

3.4 Invalid State

When $S = R = 1$, both outputs Q and Q' become 0 (violates $Q' = \overline{Q}$).

4 NAND-based SR Latch (Active-Low Inputs)

4.1 Structure

Two NAND gates with feedback.

4.2 Inputs

- \overline{S} (Set) – Active-low (0 sets $Q = 1$)
- \overline{R} (Reset) – Active-low (0 resets $Q = 0$)

4.3 Truth Table

\overline{S}	\overline{R}	Q	Q'	State
1	1	Q	Q'	Hold (Memory)
0	1	1	0	Set ($Q = 1$)
1	0	0	1	Reset ($Q = 0$)
0	0	1	1	Invalid (Race)

4.4 Invalid State

When $\overline{S} = \overline{R} = 0$, both outputs Q and Q' become 1 (violates $Q' = \overline{Q}$).

5 Characteristics

- **Level-Triggered:** Changes state based on input levels (not edges).
- **Asynchronous:** No clock signal required.
- **Race Condition:** Occurs when both inputs are active simultaneously.

6 Applications

- Basic memory storage in registers.
- Debouncing switches.
- Temporary state storage in control circuits.

7 Limitations

- **No Clock Control:** Cannot synchronize with a clock (unlike flip-flops).
- **Glitches:** Sensitive to input changes.
- **Invalid State:** Must avoid $S = R = 1$ (NOR) or $\overline{S} = \overline{R} = 0$ (NAND).

8 Conclusion

The **SR Latch** is the simplest sequential circuit used for **1-bit storage**. It has two stable states (**Set & Reset**) but suffers from an **invalid state** when both inputs are active. It serves as the foundation for more complex storage elements like **Flip-Flops**.